

< Summary of lumped equivalent circuit >

①

Complex impedance Z_f

$$Z_f = \frac{1}{Z_{dc}} + \frac{1}{Z_b}, \quad Z_f = \frac{Z_b Z_{dc}}{Z_b + Z_{dc}} \quad \dots (1)$$

where

$$Z_b = R_b + \frac{1}{i\omega C} \quad : \quad C \text{ is capacitance}$$

$$\text{Let } m = \frac{R_{dc}}{R_{dc} + R_b} \quad \text{and} \quad T = (R_b + R_{dc}) C$$

$$\text{Then } Z_f = R_{dc} - R_{dc} \cdot m \left(1 - \frac{1}{i\omega C} \right)$$

Note...

This is the same form of Cole-Cole model with $C=1$.

$$\checkmark \text{ Frequency effect (FE)} = \frac{Z_{f \min} - Z_{f \max}}{Z_{f \max}}$$

$$\text{Assume } Z_{f \min} = R_{dc} \quad \& \quad Z_{f \max} = Z_f$$

$$\text{FE} = \frac{R_{dc}}{R_b}$$

$$R_b \downarrow \rightarrow \text{FE} \uparrow$$

More conductive FE increase

✓ Time domain effect (step-off)

$$V_t \equiv V_s(t) = V_p \left[\frac{R_{dc}}{R_{dc} + R_b} \right] e^{-t/\tau}$$

where $V_p = I R_{dc}$ & $V_t = [I Z_f]$

$\hat{\mathcal{L}}^{-1} \rightarrow$ Laplace transform operator

Define chargeability M' as V_t at $t=0$


$$M' = \frac{V_s}{V_p} = \frac{R_{dc}}{R_{dc} + R_b} = m$$

Thus,

$$FE = \frac{R_{dc}}{R_b} = \frac{m}{1-m} \approx \frac{m}{1+m} \quad ??$$

$$\sigma_0 < \sigma_{\infty}$$


$$\rho_0 > \rho_{\infty}$$

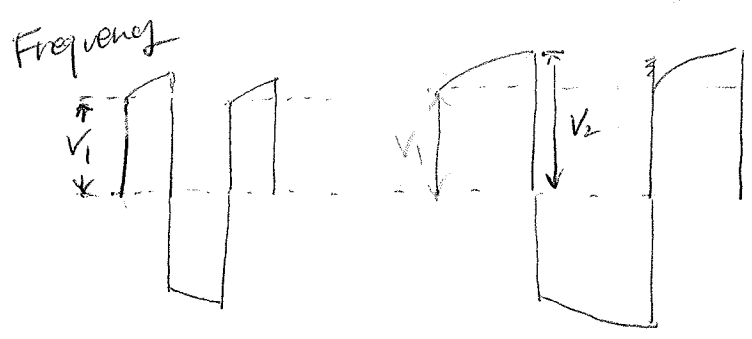

$$f=0, f=\infty$$

$$\Delta V = V_2 - V_1$$

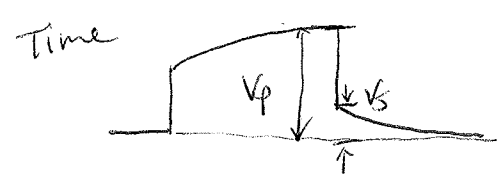
$$FE = \frac{V_2 - V_1}{V_{avg}} \quad ??$$



$$\textcircled{M} = \frac{V_s}{V_p} \leftrightarrow \frac{\Delta V}{V_2}$$

Define chargeability as
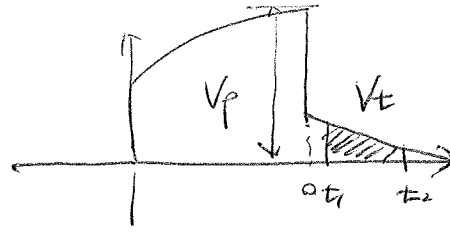
$$M^2 = \frac{1}{V_p} \int_{t_1}^{t_2} V_t dt$$



$$M^2 = m \int_0^{\infty} e^{-\frac{1}{T}t} dt = mT = \underline{\underline{Rdc C}}$$

$$\therefore \text{Thus } m = M' \neq \underline{\underline{M^2 \approx mT}}$$

M^2 is measure of C , capacitance